



SISTEME CU CIRCUITE INTEGRATE DIGITALE

Proiect automat secvential

Proiect realizat de: Achiriloaei Ioana-Isabela


Seria: A

Grupa: 2123

Indrumator: Asistent universitar Ing.Bianca Bota

CERINTE:

 Sa se proiecteze un automat secvențial corespunzător cu diagrama de stări din figura de mai jos.




1. Proiectarea circuitului utilizând multiplexoare 2:1 și numărător 74163.
2. Descrierea structurală al automatului.
3. Descrierea comportamentală al automatului.
4. Modul de verificare, in care sunt generate semnale de control astfel încât automatul sa parcurgă toate stările posibile din diagramă.

Proiectarea circuitului:


Pentru a proiecta circuitul se va completa un tabel de adevar corespunzator automatului unde trecem valorile starilor urmatoare in functie de starea curenta și de semnalele de control. Rezultatele sunt trecute in tabelul de mai jos.

QC	QB	QA	ACTIUNE	Ld	Pt	C	B	A
0	0	0	numara	1	1	x	x	x
0	0	1	incarca	0	x	0	1	1
0	1	0	incarca	0	x	0	0	0
0	1	1	numara	1	x	x	x	x
1	0	0	incarca	0	x	1	1	0
1	0	1	incarca	0	x	0	0	0
1	1	0	incarca+numara	a	1	0	0	1
1	1	1	mentine+incarca	\bar{b}	0	0	0	0

 Cu ajutorul valorilor obtinute in tabelul de mai sus, putem completa schema logica realizata din numaratorul 74163 si cele 11 muxuri 2:1



Qc	Qb	Qa	Ld	Pt	e	A	A
0	0	0	1	1	X	X	X
0	0	1	0	X	0	1	1
0	1	0	0	X	0	0	0
0	1	1	1	1	X	X	X
1	0	0	0	X	1	1	0
1	0	1	0	X	0	0	0
1	1	0	a	1	0	0	1
1	1	1	b	0	0	0	0

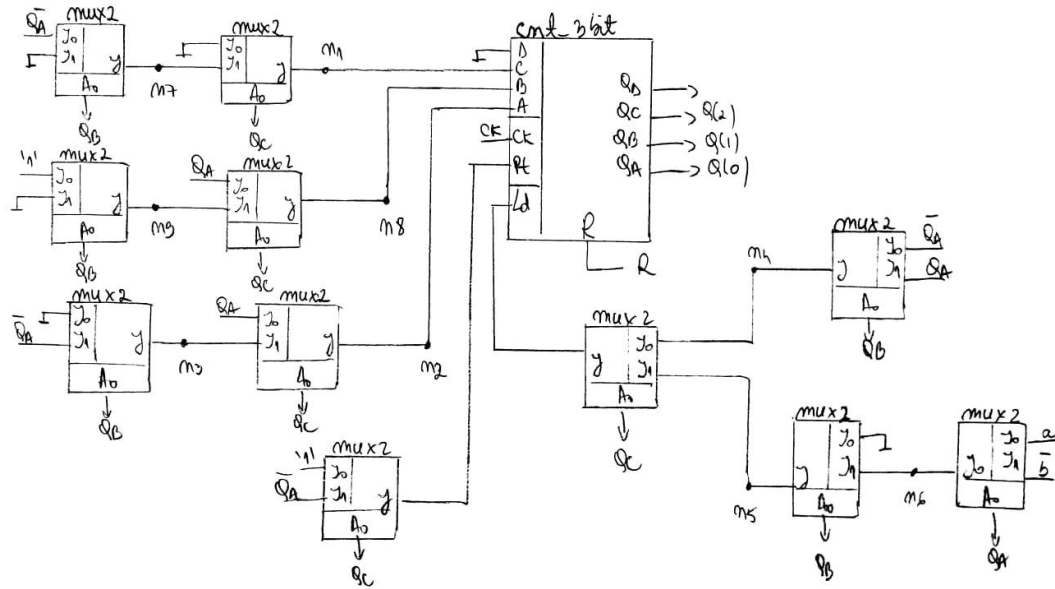

Descrierea structurala al automatului:

cnt_3bit:

```
3      library IEEE;
4      use IEEE.STD_LOGIC_1164.ALL;
5      use IEEE.std_logic_signed.all;
6
7      entity cnt3bit is
8          Port ( ck : in STD_LOGIC;
9                Pt : in STD_LOGIC;
10               Ld : in STD_LOGIC;
11               R : in STD_LOGIC;
12               D : in STD_LOGIC_VECTOR( 2 downto 0);
13               Q : out STD_LOGIC_VECTOR(2 downto 0)
14             );
15
16      end cnt3bit;
17
18      architecture Behavioral of cnt3bit is
19          signal stare : STD_LOGIC_VECTOR(2 downto 0);
20          begin
21              Q <= stare;
22              cnt3bit: process (ck)
23              begin
24                  if R = '0' then stare <= "000";
25                  elsif rising_edge(ck) then
26                      if Ld='0' then
27
28                          stare <= D;
29                      else
30                          if Pt='0' then
31                              stare <= stare;
32                          else
33                              stare <= stare+1;
34                          end if;
35                      end if;
36                  --end if;
37              end if;
38          end process;
39      end Behavioral;
```

mux 2:1

```
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4
5  entity mux_2 is
6      Port ( A : in STD_LOGIC;
7            I : in STD_LOGIC_VECTOR(0 to 1);
8            Y : out STD_LOGIC);
9  end mux_2;
10
11 architecture Behavioral of mux_2 is
12
13 begin
14     mux2: process (A,I)
15     begin
16         case A is
17             when '0' => Y <= I(0);
18             when '1' => Y <= I(1);
19             when others => Y <= 'X';
20         end case;
21     end process;
22
23 end Behavioral;
```

inversor:

```
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 entity invs is
26     Port ( x : in STD_LOGIC;
27           f : out STD_LOGIC);
28 end invs;
29
30 architecture Behavioral of invs is
31
32 begin
33     f<= not x;
34
35 end Behavioral;
```

interconectare:

```
4  use IEEE.STD_LOGIC_1164.ALL;
5
6
7  entity interconectare is
8      Port ( ck : in STD_LOGIC;
9            R : in STD_LOGIC;
10           a : in STD_LOGIC;
11           b : in STD_LOGIC;
12           Q : out STD_LOGIC_VECTOR (2 downto 0));
13 end interconectare;
14
15 architecture Behavioral of interconectare is
16 component cnt3bit is
17     Port ( ck : in STD_LOGIC;
18           Pt : in STD_LOGIC;
19           Ld : in STD_LOGIC;
20           R : in STD_LOGIC;
21           D : in STD_LOGIC_VECTOR( 2 downto 0);
22           Q : out STD_LOGIC_VECTOR(2 downto 0)
23           );
24 end component;
25
26 component mux_2 is
27     Port ( A : in STD_LOGIC;
28           I : in STD_LOGIC_VECTOR(0 to 1);
29           Y : out STD_LOGIC);
```

```

30     end component;
31
32     component invs is
33         Port ( x : in STD_LOGIC;
34               f : out STD_LOGIC);
35     end component;
36
37     signal Qa,Qb,Qc,Pt,Ld,Qan,Qbn,bn,an,n1,n2,n3,n4,n5,n6,n7,n8,n9 : std_logic;
38 begin
39     Q<=Qc&Qb&Qa;
40     Qan<=not Qa;
41     Qbn<=not Qb;
42     an<=not a;
43     bn<=not b;
44
45     u1: cnt3bit port map(
46         ck=>ck,
47         R=>R,
48         Ld=>Ld,
49         Pt=>Pt,
50         D(0)=>n2,
51         D(1)=>Qbn,
52         D(2)=>n1,
53         Q(0)=>Qa,
54
55         Q(1)=>Qb,
56         Q(2)=>Qc
57     );
58     u2: mux_2 port map(
59         I(0)=>'0',
60         I(1)=>n7,
61         A=>Qc,
62         Y=>n1
63     );
64     u3: mux_2 port map(
65         I(0)=>Qan,
66         I(1)=>'0',
67         A=>Qb,
68         Y=>n7
69     );
70     u4: mux_2 port map(
71         I(0)=>Qa,
72         I(1)=>n9,
73         A=>Qc,
74         Y=>n8
75     );
76     u5: mux_2 port map(
77         I(0)=>'1',

```

```

78         I(1)=>'0',
79         A=>Qb,
80         Y=>n9
81     );
82
83     u6: mux_2 port map(
84         I(0)=>Qa,
85         I(1)=>n3,
86         A=>Qc,
87         Y=>n2
88     );
89
90     u7: mux_2 port map(
91         I(0)=>'0',
92         I(1)=>Qan,
93         A=>Qb,
94         Y=>n3
95     );
96
97     u8: mux_2 port map(
98         I(0)=>'1',
99         I(1)=>Qan,
100        A=>Qc,
101        Y=>Pt

```

```

102    );
103    u9: mux_2 port map(
104        I(0)=>n4,
105        I(1)=>n5,
106        A=>Qc,
107        Y=>Ld
108    );
109    u10: mux_2 port map(
110        I(0)=>Qan,
111        I(1)=>Qa,
112        A=>Qb,
113        Y=>n4
114    );
115    u11: mux_2 port map(
116        I(0)=>'0',
117        I(1)=>n6,
118        A=>Qb,
119        Y=>n5
120    );
121    u12: mux_2 port map(
122        I(0)=>a,
123        I(1)=>bn,
124        A=>Qa,
125        Y=>n6

```

```

126    );
127 end Behavioral;
--

```


Descrierea comportamentala al automatului:

Automat_ref are scopul de a descrie comportamentul circuitului, iar la final acest semnal trebuie sa fie identic cu semnalul automatului proiectat.

automat_ref:

```
4      use IEEE.STD_LOGIC_1164.ALL;
5
6
7
8      entity automat_ref is
9          Port ( ck : in STD_LOGIC;
10              R : in STD_LOGIC;
11              a : in STD_LOGIC;
12              b : in STD_LOGIC;
13              Q_ref : out std_logic_vector(2 downto 0));
14      end automat_ref;
15
16      architecture Behavioral of automat_ref is
17          signal current_state, next_state: std_logic_vector(2 downto 0);
18      begin
19          registrare:
20          process (ck)
21          begin
22              if R = '0' then
23                  current_state <= "000";
24              elsif rising_edge(ck) then
25                  current_state <= next_state;
26              end if;
27          end process;
28          selectie:
29          process (current_state, a, b)
```

```

30 begin
31   case current_state is
32   when "000" => next_state <= "001";
33   when "001" => next_state <= "011";
34   when "011" => next_state <= "100";
35   when "100" => next_state <= "110";
36   when "110" => if a='1' then
37     next_state <= "111";
38   else
39     next_state <="001";
40   end if;
41   when "111" => if b='1' then
42     next_state <= "000";
43   else
44     next_state <= "111";
45   end if;
46
47   when "010" => next_state <= "000";
48   when "101" => next_state <= "000";
49   when others => next_state <= "001";
50
51   end case;
52   end process;
53   Q_ref <= current_state;
54 end Behavioral;

```

testbench:

```

3   library IEEE;
4   use IEEE.STD_LOGIC_1164.ALL;
5
6
7   entity test_bench is
8   -- Port ( );
9   end test_bench;
10
11  architecture Behavioral of test_bench is
12
13  component interconnectare is
14    Port ( ck : in STD_LOGIC;
15          R : in STD_LOGIC;
16          a : in STD_LOGIC;
17          b : in STD_LOGIC;
18          Q : out STD_LOGIC_VECTOR (2 downto 0));
19  end component;
20
21  component automat_ref is
22    Port ( ck : in STD_LOGIC;
23          R : in STD_LOGIC;
24          a : in STD_LOGIC;
25          b : in STD_LOGIC;
26          Q_ref : out std_logic_vector(2 downto 0));

```

```

27     end component;
28
29
30     signal ck, R, a, b : std_logic;
31     signal Q, Q_ref : std_logic_vector(2 downto 0);
32
33
34     begin
35
36         gen_R: process
37         begin
38             R <= '0';
39             wait for 5 ns;
40             R <= '1';
41             wait for 10000 ns;
42         end process;
43
44         gen_a: process
45         begin
46
47             a <= '0';
48             wait for 50 ns;
49             a <= '1';
50             wait for 50 ns;
51
52         end process;
53
54         gen_b: process
55         begin
56
57             b <= '0';
58             wait for 70 ns;
59             b <= '1';
60             wait for 70 ns;
61
62         end process;
63
64         gen_ck: process
65         begin
66             ck <= '0';
67             wait for 2ns;
68             ck <= '1';
69             wait for 2ns;
70         end process;


```

```

71 |
72 | automat1: interconectare port map(ck=>ck, a=>a, b=>b, Q=>Q, R => R);
73 | automat2: automat_ref port map(ck=>ck, a=>a, b=>b, Q_ref=>Q_ref, R => R);
74 |
75 |
76 |     verificare: process (Q)
77 |     begin
78 |         if Q /= q_ref then
79 |             report "Rezultat diferit";
80 |         end if;
81 |     end process;
82 |
83 | end Behavioral;

```

Modul de verificare:

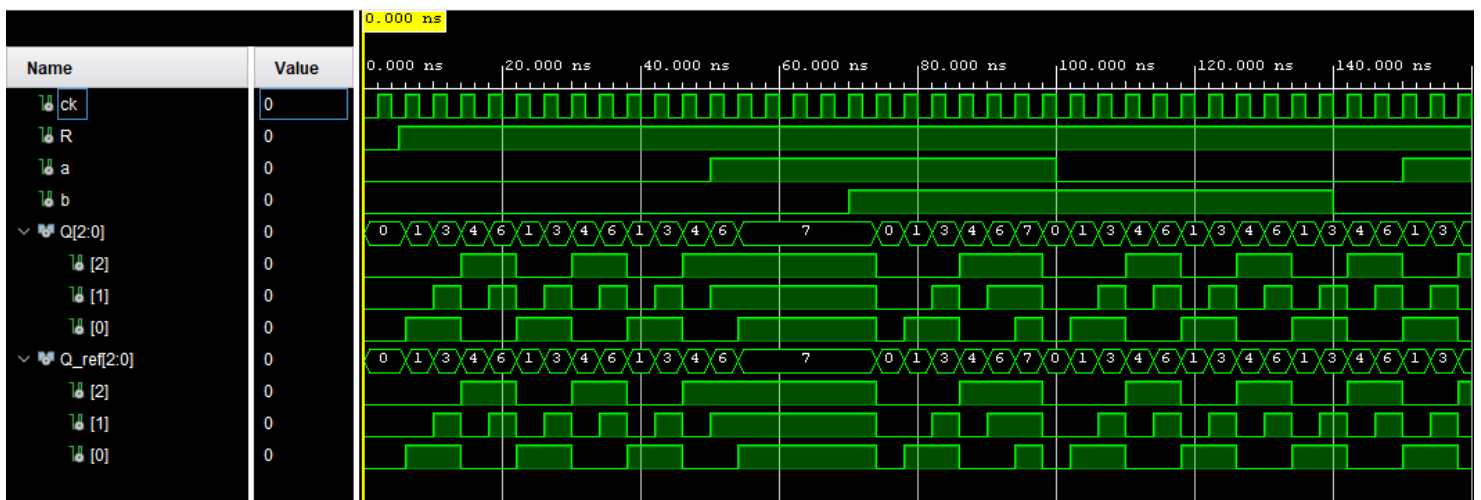

Dupa cum reiese si din diagrama ilustrata mai sus, cele doua automate sunt identice fiind parcurse toate starile.

Cand $a=0$ si $b=0$, pornesc din starea "000" dupa care numar pana in "001", apoi automatul incarca "011" care ulterior va numara starea "100" si va incarca "110", pe acest front a este in continuare 0, deci va merge in starea "001" care se va repeta pana cand a devine '1' si va trece in starea "111" unde aceasta stare va fi mentinuta cat timp b este '0', in momentul in care b va deveni '1', atunci automatul va trece in starea "000" unde automatul va parcurge starile din nou.